

1.18

$$P_1 = 30V \times (-10A) = -300W$$

$$P_2 = 10V \times 10A = 100W$$

$$P_3 = 20V \times 14A = 280W$$

$$P_4 = 8V \times (-4A) = -32W$$

$$P_5 = 12V \times (-4A) = -48W$$

1.20

$$\text{电源的功率 } P_0 = 30V \times (-6A) = -180W$$

$$12V \text{ 元件功率 } P_1 = 12V \times 6A = 72W$$

$$2A \text{ 电流流经的 } 28V \text{ 元件 } P_2 = 28V \times 2A = 56W$$

$$1A \text{ 电流流经的 } 28V \text{ 元件 } P_3 = 28V \times 1A = 28W$$

$$\text{受控电压源 } P_4 = 5I_2 \times (-3A) = 5 \times 2 \times -3 = -30W$$

由于所有元件功率代数和为0, 设 V_0 元件的功率为 P_5

$$\text{则 } P_1 + P_2 + P_3 + P_4 + P_5 = -54 + P_5 = 0, \text{ 可得 } P_5 = 54W$$

$$\text{又由 } V_0 \times 3A = P_5, \text{ 可得 } V_0 = 18V,$$

1.23

$$W = P_t = 1.8 \times \frac{15}{60} \times 30 \text{ kW} \cdot \text{h} = 13.5 \text{ kW} \cdot \text{h}$$

$$C = 10 \times 13.5 = 135 \text{ 美分} = 1.35 \text{ 美元}$$

1.36

$$(a) \quad I_{\max} = 20 \div \left(\frac{15}{60}\right) = 20 \div 0.25 = 80A$$

$$(b) \quad (20/0.002) \div 24 = 416.7 \text{ (天)}$$