

第七章作业

7.44

① $t < 0$ 时, 电路已稳态, 电容视为开路, 右侧电容支路无电流

$$\text{则 } i(0) = \frac{30}{6+3} = \frac{10}{3} \text{ A}, \quad V_C(0) = i(0) \cdot 3 = 10 \text{ V},$$

$$V_C(0^+) = V_C(0) = 10 \text{ V}$$

② $t \rightarrow \infty$ 时, 电路也已稳态, 则 $i(\infty) = \frac{60}{6+3} = \frac{20}{3} \text{ A}, \quad V_C(\infty) = i(\infty) \cdot 3 = \frac{20}{3} \times 3 = 20 \text{ V}$

$$\text{又由 } R_{eq} = 6 \parallel 3 = 2 \Omega, \quad \tau = R_{eq} C = 2 \times 2 = 4 \text{ s}$$

$$\text{由 } v(t) = V(\infty) + [V(0) - V(\infty)] e^{-\frac{t}{\tau}}, \text{ 代入得,}$$

$$v(t) = 20 - 10 e^{-\frac{t}{4}} \quad (t > 0)$$

$$\text{又由 } i(t) = C \frac{dv}{dt}, \text{ 代入得}$$

$$i(t) = 2 \times \frac{10}{4} e^{-\frac{t}{4}} = 5 e^{-\frac{t}{4}} \text{ A}, \quad t > 0$$

7.48

① $t < 0$ 时, 由单位阶跃函数定义, 有 $u(-t) = 1$,

$$\text{则 } v(0) = 1 \times 10 = 10 \text{ V}, \quad v(0^+) = v(0) = 10 \text{ V},$$

② $t \rightarrow \infty$ 时, 由单位阶跃函数定义, 有 $u(-t) = 0$,

$$\text{则 } v(\infty) = 0$$

$$\text{且 } R_{eq} = 20 + 10 = 30 \Omega, \quad \tau = R_{eq} C = 30 \times 0.1 = 3 \text{ s}$$

$$\text{由 } v(t) = v(\infty) + [v(0) - v(\infty)] e^{-\frac{t}{\tau}}, \text{ 代入得}$$

$$v(t) = 10 e^{-\frac{t}{3}}, \quad (t > 0)$$

$$\text{又由 } i(t) = C \frac{dv}{dt}, \text{ 代入得}$$

$$i(t) = 0.1 \times -\frac{10}{3} e^{-\frac{t}{3}} = -\frac{1}{3} e^{-\frac{t}{3}} \text{ A},$$

$$\text{则 } \begin{cases} v(t) = 10 e^{-\frac{t}{3}}, & t > 0 \\ i(t) = -\frac{1}{3} e^{-\frac{t}{3}}, & t > 0 \end{cases}$$

7.49

$$\text{由 } R_{eq} = 6 + 4 = 10 \Omega, \quad \text{则 } \tau = R_{eq} C = 10 \times 0.5 = 5 \text{ s}$$

① $0 \leq t < 1$ 时, 由 $v(0) = 0$, 达到稳态时, 电容开路,

$$\text{则 } v(\infty) = 2 \times 4 = 8 \text{ V}$$

$$\text{则 } v(t) = v(\infty) + [v(0) - v(\infty)] e^{-\frac{t}{\tau}} = 8 + (-8) e^{-\frac{t}{5}} = 8(1 - e^{-\frac{t}{5}}) \text{ V}, \quad 0 \leq t < 1.$$

② $t \geq 1$ 时, 由 $v(1) = 8(1 - e^{-\frac{1}{5}}) = 1.45$, 则 $v(1^+) = v(1) = 1.45 \text{ V}$

达到稳态时, $v(\infty) = 0 \text{ V}$,

$$\text{则 } v(t) = v(\infty) + [v(1) - v(\infty)] e^{-\frac{t-1}{\tau}} = 1.45 e^{-\frac{t-1}{5}} \text{ V}, \quad t \geq 1$$

因此

$$v(t) = \begin{cases} 8(1 - e^{-\frac{t}{5}}) \text{ V}, & 0 \leq t < 1 \\ 1.45 e^{-\frac{t-1}{5}} \text{ V}, & t \geq 1 \end{cases}$$

7.53

(a)

① $t < 0$ 时, 电路达到稳态时, $i(0^-) = \frac{25}{3+1} = 5A$,则 $i(t) = i(0^-) = 5A, t < 0$ ② $t > 0$ 时, $i(0^+) = i(0^-) = 5A, R_{eq} = 2\Omega, \tau = \frac{L}{R_{eq}} = \frac{4}{2} = 2s$,则 $i(t) = i(0^+)e^{-\frac{t}{\tau}} = 5e^{-\frac{t}{2}}A$,即 $i(t) = \begin{cases} 5A, & t < 0 \\ 5e^{-\frac{t}{2}}, & t > 0 \end{cases}$

(b)

① $t < 0$ 时, 电路达到稳态时, $i(0^-) = 6A$, 则 $i(t) = i(0^-) = 6A, t < 0$.② $t > 0$ 时, $i(0^+) = i(0^-) = 6A, R_{eq} = 2\Omega, \tau = \frac{L}{R_{eq}} = \frac{3}{2}s$,则 $i(t) = i(0^+)e^{-\frac{t}{\tau}} = 6e^{-\frac{2}{3}t}A, t > 0$ 即 $i(t) = \begin{cases} 6A, & t < 0 \\ 6e^{-\frac{2}{3}t}A, & t > 0 \end{cases}$

7.56

 $R_{eq} = 6 + 20 \parallel 5 = 10\Omega, \tau = \frac{L}{R_{eq}} = 0.05s$,而 $i(0)$ 可由 KCL 得到, 对与分支路交汇的节点应用 KCL:

$$2 + \frac{20 - V_x}{5} = \frac{V_x}{12} + \frac{V_x}{20} + \frac{V_x}{6}, \text{ 可得 } V_x = 12V,$$

则 $i(0) = \frac{V_x}{6} = 2A$,又由 $20 \parallel 5 = 4, i(\infty) = \frac{4}{4+6} \times 4 = 1.6A$, $i(t) = i(\infty) + [i(0) - i(\infty)]e^{-\frac{t}{\tau}}$, 代入得:

$$i(t) = 1.6 + (2 - 1.6)e^{-\frac{t}{0.05}} = 1.6 + 0.4e^{-20t},$$

又由 $v(t) = L \frac{di}{dt}$, 代入得:

$$v(t) = \frac{1}{2} \times 0.4 \times -20 \times e^{-20t} = -4e^{-20t}V, t > 0$$