

课堂作业整理 3.17

例 3.1

$$\begin{cases} \frac{V_1}{2} = 5 + \frac{V_1 - V_2}{4} \\ \frac{V_1 - V_2}{4} + 10 = \frac{V_2}{6} + 5 \end{cases} \quad \text{解} \quad \begin{cases} V_1 = 13.3V \\ V_2 = 20V \end{cases}$$

练 3.1

$$\begin{cases} 14 = \frac{V_1}{4} + \frac{V_1 - V_2}{5} \\ \frac{V_1 - V_2}{5} = \frac{V_2}{5} + 7 \end{cases} \quad \text{解} \quad \begin{cases} V_1 = 30V \\ V_2 = -2.5V \end{cases}$$

例 3.2

$$\begin{cases} i_1 + i_x = 3 \\ i_x = i_2 + i_3 \\ i_1 + i_2 = 2i_x \\ i_1 = \frac{V_1 - V_2}{4} \\ i_x = \frac{V_1 - V_2}{2} \\ i_2 = \frac{V_2 - V_3}{2} \\ i_3 = \frac{V_2}{4} \end{cases} \quad \text{解} \quad \begin{cases} V_1 = 4.8V \\ V_2 = 2.4V \\ V_3 = -2.4V \end{cases}$$

练 3-2

$$\begin{cases} \frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{2} = 4 \\ \frac{V_2}{4} = \frac{V_1 - V_2}{3} + 4 \times \frac{V_2}{4} \\ \frac{V_3}{6} + 4 \times \frac{V_2}{4} = \frac{V_1 - V_3}{2} \end{cases} \quad \text{解} \quad \begin{cases} V_1 = 32V \\ V_2 = -25.6V \\ V_3 = 62.4V \end{cases}$$

例 3-3

$$\text{KCL: } V_2 = -20 - 2V_1$$

$$\text{KVL: } V_2 = V_1 + 2$$

$$\Rightarrow \begin{cases} V_1 = -7.33V \\ V_2 = -5.33V \end{cases}$$

练 3-3

$$\begin{cases} 2i - V = 6 \\ \frac{14 - V}{4} = \frac{V}{3} + i + \frac{2i}{6} \end{cases} \quad \Rightarrow \quad \begin{cases} V = -400mV \\ i = 2.8A \end{cases}$$