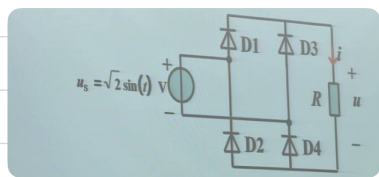


课堂笔记整理 4.17

AC-DC 转换





此时无电容, 仅两种情况:

① $D1$ 与 $D4$ 导通: 此时 $u_s > 0$, $D2, D3$ 截止,
 $u = u_s$

② $D2$ 与 $D3$ 导通: 此时 $u_s < 0$, $D1, D4$ 截止,
 $u = -u_s$


因此电压波形 $u = |u_s|$, 近似于

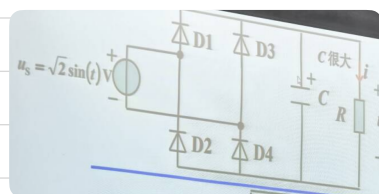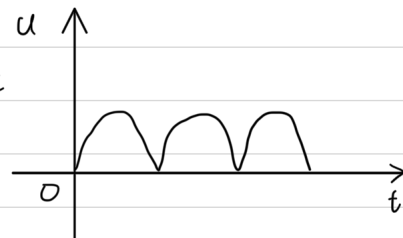

这时负载并联了电容,

① $u_s > 0$ 时, $D1$ 与 $D4$ 导通, 先给 C 充电, 当电压下降时
就放电, 由于放电缓慢, 会比正弦波更平缓

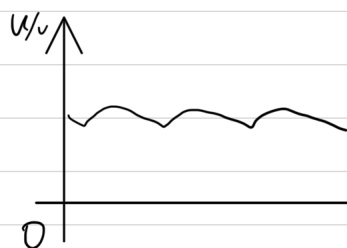② $u_s < 0$ 时, $D2$ 与 $D3$ 导通, 同样地, 电压上升时给电
容充电, 电压减小时放电



可以看到并联电容后波形更平滑, 起到了滤波作用.

练 8-2

(a) $i_L(0^+) = i_L(0^-) = -6A$, $V_L(0^+) = V_L(0^-) = 0V$, $V_R(0^+) = i_R(0^+)R = (i_L(0^+) + 6)R = 0 \times R = 0V$

(b) $\frac{di_L(0^+)}{dt} = \frac{V_L(0^+)}{L} = \frac{0}{2} = 0$, 由 KVL: $V_L(0^+) + V_R(0^+) + V_C(0^+) = 0$,

即 $V_L(0^+) = 0$, $\frac{dV_L(0^+)}{dt} = \frac{i_L(0^+)}{C} = \frac{4}{0.2} = 20V/s$,

由 KCL: $i_L(0^+) = 4 - i_R(0^+) = 4 - (6 + i_L(0^+)) = 4 - 0 = 4A$,

$\frac{di_R(0^+)}{dt} = \frac{d(6 + i_L(0^+))}{dt} = \frac{di_L(0^+)}{dt} = 0$, $\frac{dV_R(0^+)}{dt} = R \frac{di_R(0^+)}{dt} = 5 \times 0 = 0$

(c) $i_L(\infty) = 2A$, $V_L(\infty) = 20V$, $V_R(\infty) = 20V$