

课堂笔记整理 4.7

7.2 节

例 7-1

$$R_{eq} = 20 \parallel 15 = 4 \Omega, \quad \tau = R_{eq}C = 4 \times 0.1 = 0.4s,$$

$$v = v(0)e^{-\frac{t}{\tau}} = 15e^{-\frac{t}{0.4}} V, \quad \text{则 } v_c = v = 15e^{-2.5t} V$$

$$v_x = \frac{12}{12+8} v = 0.6 \times (15e^{-2.5t}) = 9e^{-2.5t} V$$

$$i_x = \frac{v_x}{12} = 0.75e^{-2.5t} V$$

练 7-1

$$R_{c6112} = 6 \parallel 12 = 4 \Omega, \quad R_{eq} = 8 + 4 = 12 \Omega$$

$$\tau = R_{eq}C = 12 \times \frac{1}{3} = 4s, \quad v_c = v(0)e^{-\frac{t}{\tau}} = 60e^{-0.25t}$$

$$v_x = \frac{4}{4+8} v_c = \frac{1}{3} \times 60 \times e^{-\frac{t}{4}} = 20e^{-0.25t}, \quad i_c = -\frac{v_c}{R_{eq}} = -5e^{-0.25t}$$

例 7-2

$$v_c(t) = \frac{9}{9+3} 20 = 15V, \quad R_{eq} = 1+9 = 10\Omega, \quad \tau = R_{eq}C = 10 \times 20 \times 10^{-3} = 0.2s$$

$$v(t) = v_c(0)e^{-\frac{t}{\tau}} = 15e^{-\frac{t}{0.2}} = 15e^{-5t} V, \quad w_c(0) = \frac{1}{2} C v_c^2(0) = \frac{1}{2} \times 20 \times 10^{-3} \times 15^2 = 2.25J$$

练 7-2

$$R_{eq} = 4 \parallel 12 = 3\Omega, \quad v_c(0) = \frac{3}{9} \times 24 = 8V, \quad \tau = R_{eq}C = 3 \times \frac{1}{6} = 0.5s$$

$$v = 8e^{-\frac{t}{\tau}} = 8e^{-2t} V, \quad w_0 = \frac{1}{2} C v^2 = \frac{1}{2} \times \frac{1}{6} \times 8^2 = 5.33J$$

7.3 节

例 7-3

可列得如下方程:

$$\begin{cases} 2(i_1 - i_2) + \frac{1}{2} \frac{di_1}{dt} = 0 \\ -3i_1 + 4i_2 + 2(i_2 - i_1) = 0 \\ i_1 = i_2 \end{cases}$$

$$\text{整理后可得 } \frac{di_1}{dt} + \frac{2}{3} i_1 = 0, \quad \text{即 } \frac{di_1}{i_1} = -\frac{2}{3} dt$$

$$\text{又对等式两边积分, 得: } \ln i_1 \Big|_{i(0)}^{i(t)} = -\frac{2}{3} t \Big|_0^t, \quad \text{即 } \ln \frac{i(t)}{i(0)} = -\frac{2}{3} t.$$

$$\text{即 } i(t) = i(0)e^{-\frac{2}{3}t} = 10e^{-\frac{2}{3}t} A,$$

$$\text{故 } v = L \frac{di}{dt} = 0.5 \times 10 \times (-\frac{2}{3}) e^{-\frac{2}{3}t} = -\frac{10}{3} e^{-\frac{2}{3}t} V$$

$$\text{则 } i_x(t) = \frac{v}{2} = -1.667 e^{-\frac{2}{3}t} A$$

练 7-3

$$-1 + v_x + 6 \times i_2 = 0, \quad -2v_x + 2(i_2 - i_1) + 6 \times i_2 = 0, \quad v_x = 1 \times i_1,$$

$$i_1 = \frac{1}{4}, \quad i_2 = \frac{1}{8}, \quad R_{eq} = \frac{1}{\frac{1}{4}} = 4\Omega, \quad \tau = \frac{L}{R} = \frac{2}{4} = 0.5s$$

$$\text{则 } i(t) = 7e^{-2t} A, \quad t > 0, \quad v_x = -1 \times 1 = -7e^{-2t} A, \quad t > 0.$$

例 7-4

$$4 \parallel 12 = 3\Omega, \quad I_x = \frac{40}{2+3} = 8A, \quad I_0 = \frac{12}{12+4} \times 8 = 6A,$$

$$R_{eq} = 16 \parallel 16 = 8\Omega, \quad \tau = \frac{L}{R} = \frac{2}{8} = \frac{1}{4}, \quad i(t) = I_0 e^{-\frac{t}{\tau}} = 6e^{-4t}$$

练7-4

$t < 0$ 时, 电感短路, 即 5Ω 电阻两端视作开路, $8 \parallel 24 = 6\Omega$

$$I_0 = \frac{6}{6+12} \times 6 = 2A, \quad R_{eq} = (8+2) \parallel 5 = 4\Omega, \quad \tau = \frac{L}{R} = \frac{2}{4} = 0.5$$

$t > 0$ 时,

$$i(t) = I_0 e^{-\frac{t}{\tau}} = 2e^{-2t} A$$

例7-5

$t < 0$ 时, $i_0 = 0$, $i(t) = \frac{10}{2+3} = 2A, t < 0$, $V_0(t) = 3i(t) = 6V, t < 0$

$t > 0$ 时, $R_{Th} = 3 \parallel 6 = 2\Omega$, $\tau = \frac{L}{R_{Th}} = 1s$, $i(t) = i(0)e^{-\frac{t}{\tau}} = 2e^{-t} A, t > 0$

$$V_0(t) = -V_L = -L \frac{di}{dt} = -2(-2e^{-t}) = 4e^{-t} V, t > 0$$

$$i_0(t) = \frac{V_0}{6} = -\frac{2}{3}e^{-t} A, t > 0$$

练7-5

$t < 0$ 时,

$$i = \frac{4}{6} \times 24 = 16A, \quad V_0 = 16 \times 2 = 32V, \quad i_0 = \frac{2}{6} \times 24 = 8A$$

$t \geq 0$ 时,

$$R_{eq} = (4+2) \parallel 3 = 2\Omega, \quad \tau = \frac{L}{R} = \frac{1}{2}, \quad i(t) = 16e^{-2t} A$$

$$V_L(t) = L \times \frac{di}{dt} = 1 \times 16 \times (-2)e^{-2t} = -32e^{-2t} V$$

$$i_3(t) = -\frac{32}{3} \times e^{-2t} A, \quad i_0(t) = -(i_3(t) + i(t)) = \frac{32}{3}e^{-2t} - 16e^{-2t} = -5.333e^{-2t} A,$$

$$V_0(t) = -2 \times i_0(t) = \frac{32}{3} \times e^{-2t} = 10.667e^{-2t} V$$

$$\text{则 } i = \begin{cases} 16A, & t < 0 \\ 16e^{-2t}, & t \geq 0 \end{cases} \quad i_0 = \begin{cases} 8A, & t < 0 \\ -5.333e^{-2t}A, & t > 0 \end{cases} \quad V_0 = \begin{cases} 32V, & t < 0 \\ 10.667e^{-2t}V, & t > 0 \end{cases}$$