

课堂笔记整理 5.19

堂练1

用网孔法, 网孔1有 $I_1 = 4A$, 网孔2有 $(j10 - j5)I_2 - j10I_1 + 60\angle 30^\circ = 0$

可解得 $I_2 = 10.58\angle 79.1^\circ A$

① 对电流源:

$$V_1 = 20I_1 + j10(I_1 - I_2) = 80 + j10(4 - 2 - j10.39) = 184.984\angle 6.21^\circ V$$

$$P_1 = -\frac{1}{2} \times 184.984 \times 4 \times \cos 6.21^\circ = -367.8 W$$

② 对电阻:

$$P_2 = \frac{1}{2} \times 80 \times 4 = 160 W$$

③ 对电容:

$$I_2 = 10.58\angle 79.1^\circ$$

$$V_4 = -j5I_2 = 5\angle -90^\circ \times 10.58\angle 79.1^\circ = 52.9\angle (-90^\circ + 79.1^\circ)$$

$$P_4 = \frac{1}{2} \times 52.9 \times 10.58 \cos(-90^\circ) = 0$$

④ 对电感:


$$I_3 = I_1 - I_2 = 2 - j10.39 = 10.58\angle -79.1^\circ$$

$$V_3 = j10(I_1 - I_2) = 105.8\angle (-79.1^\circ + 90^\circ)$$

$$P_3 = \frac{1}{2} \times 105.8 \times 10.58 \cos 90^\circ = 0$$

⑤ 对电压源:


$$P_5 = \frac{1}{2} \times 60 \times 10.58 \cos(30^\circ - 79.1^\circ) = 207.8 W$$

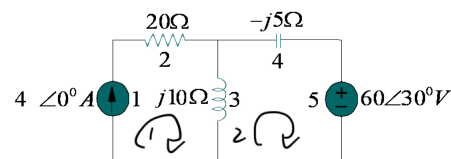

堂练2

对负载两端求戴维南等效:
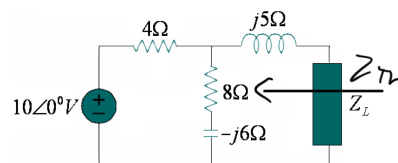
$$V_{Th} = \frac{8 - j6}{4 + 8 - j6} \times 10 = 7.454\angle -10.3^\circ V$$



$$Z_{Th} = j5 + 4 \parallel (8 - j6) = j5 + \frac{4(8 - j6)}{4 + 8 - j6} = 2.933 + j4.467 \Omega$$

$$\text{则 } P_{max} = \frac{|V_{Th}|^2}{8R_{Th}} = \frac{7.454^2}{8 \times 2.933} = 2.368 W$$

堂练3

同样求 R_L 两端戴维南等效:


$$Z_{Th} = j20 \parallel (40 - j30) = \frac{j20(40 - j30)}{j20 + 40 - j30} = 9.412 + j22.35 \Omega$$

$$V_{Th} = \frac{j20}{j20 + 40 - j30} (150\angle 30^\circ) = 72.76\angle 134^\circ V$$

$$R_L = |Z_{Th}| = \sqrt{9.412^2 + 22.35^2} = 24.25 \Omega$$

$$I = \frac{V_{Th}}{Z_{Th} + R_L} = \frac{72.76\angle 134^\circ}{33.39 + j22.35} = 1.8\angle 100.2^\circ A$$

$$P_{max} = \frac{1}{2} |I|^2 R_L = \frac{1}{2} \times 1.8^2 \times 24.25 = 39.29 W$$

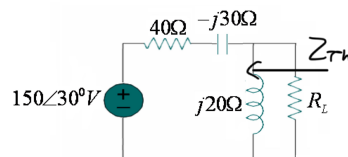

堂练4

$$(a) \quad V_{rms} = \frac{60}{\sqrt{2}} \angle -10^\circ, \quad I_{rms} = \frac{1.5}{\sqrt{2}} \angle 50^\circ$$

复功率:

$$\tilde{S} = V_{rms} I_{rms} = \frac{60}{\sqrt{2}} \angle -10^\circ \times \frac{1.5}{\sqrt{2}} \angle 50^\circ = 45 \angle -60^\circ \text{ VA},$$

视在功率为: $S = |\tilde{S}| = 45 \text{ VA}$

$$(b) \quad \text{由 } \tilde{S} = 45 \angle -60^\circ = 45 [\cos(-60^\circ) + j \sin(-60^\circ)] = 22.5 - j38.97$$

由于 $\tilde{S} = P + jQ$, 有功功率为 $P = 22.5 \text{ W}$.

无功功率为 $Q = -38.97 \text{ VAR}$

$$(c) \quad \text{功率因数为: } pf = \cos(-60^\circ) = 0.5$$

$$\text{负载阻抗为: } Z = \frac{V}{I} = \frac{60 \angle -10^\circ}{1.5 \angle 50^\circ} = 40 \angle -60^\circ \Omega$$