

第六章习题

6-11

$$\text{由 } V = \frac{1}{C} \int_0^t i dt + V_0, \quad V = 10 + \frac{1}{4 \times 10^{-3}} \int_0^t i(t) dt$$

$$\text{当 } 0 < t < 2s \text{ 时, } v(t) = 10 + \frac{10^{-3}}{4 \times 10^{-3}} \int_0^t 15 dt = 10 + 3.75t,$$


$$\text{当 } 2 < t < 4s \text{ 时, } v(t) = v(2) + \frac{10^{-3}}{4 \times 10^{-3}} \int_2^t -10 dt = 22.5 - 2.5t$$

$$\text{当 } 4 < t < 6s \text{ 时, } v(t) = v(4) + \frac{10^{-3}}{4 \times 10^{-3}} \int_4^t 0 dt = 12.5 V$$

$$\text{当 } 6 < t < 8s \text{ 时, } v(t) = v(6) + \frac{10^{-3}}{4 \times 10^{-3}} \int_6^t 10 dt = 2.5t - 2.5$$

则
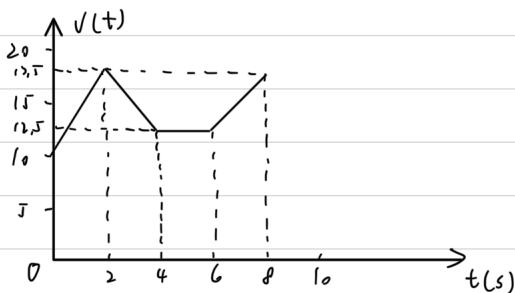
$$v(t) = \begin{cases} 10 + 3.75t \text{ V} & 0 < t < 2s \\ 22.5 - 2.5t \text{ V} & 2 < t < 4s \\ 12.5 \text{ V} & 4 < t < 6s \\ 2.5t - 2.5 \text{ V} & 6 < t < 8s \end{cases}$$



6-19

$$30 + 40 = 120 \mu F, \quad 30 + 20 + 10 = 60 \mu F, \quad 60 \parallel 60 = \frac{60 \times 60}{60 + 60} = 30 \mu F,$$

$$50 + 30 = 80 \mu F, \quad 120 \parallel 80 = \frac{120 \times 80}{120 + 80} = 48 \mu F, \quad 48 + 12 = 60 \mu F$$

$$12 \parallel 60 = \frac{12 \times 60}{12 + 60} = 10 \mu F$$

即等效电容为 $10 \mu F$

6-32

$$(a) \quad v_1(t) = v_1(0) + \frac{1}{C_1} \int_0^t i_s dt = 4.5 \times \frac{1}{12 \times 10^{-6}} \int_0^t e^{-2t} dt = 187.5(1 - e^{-2t}) \text{ V}$$

$$v_2(t) = v_2(0) + \frac{1}{C_2} \int_0^t \frac{40}{40 + 120} i_s dt = 3 \times \frac{1}{40 \times 10^{-6}} \int_0^t e^{-2t} dt = 37.5(1 - e^{-2t}) \text{ V}$$

(b) 由能量公式 $W = \frac{1}{2} C v^2(t)$, 得

$$W_{(12 \mu F)} = \frac{1}{2} C_{(12 \mu F)} v_1^2 = 210.94 (1 - e^{-2t})^2 \text{ mJ}$$

$$W_{(20 \mu F)} = \frac{1}{2} C_{(20 \mu F)} v_2^2 = 14.06 (1 - e^{-2t})^2 \text{ mJ}$$

$$W_{(40 \mu F)} = \frac{1}{2} C_{(40 \mu F)} v_2^2 = 28.13 (1 - e^{-2t})^2 \text{ mJ}$$

6-46

$$\text{由分流规律, } i_L = \frac{4}{2+4} \times 3 = 2 \text{ A}, \quad v_L = 0 \text{ V}$$

$$\text{则 } W_C = \frac{1}{2} C v_C^2 = 0 \text{ J}$$

$$W_L = \frac{1}{2} L i^2 = \frac{1}{2} \times 0.5 \times 4 = 1 \text{ J}$$

6-51

$$\frac{1}{\frac{1}{60} + \frac{1}{20} + \frac{1}{30}} = 10 \text{ mH}, \quad 10 + 25 = 35 \text{ mH}.$$

$$\text{则 } L_{eq} = \frac{10 \times 35}{10 + 35} = 7.778 \text{ mH}$$